 


CSCI241 – Homework #4 (Logic Gates)

Name: Alexander Antoun

74LS00 – Quad 2-input NAND Gate



Truth Tables:

Gate #1

Input A (Pin 1)	Input B (Pin 2)	Output Y (Pin 3)
LOW	LOW	HIGH, 5.14 v
LOW	HIGH	HIGH, 5.14 v
HIGH	LOW	HIGH, 5.14 v
HIGH	HIGH	LOW, 0.00 v

Gate #2

Input A (Pin 4)	Input B (Pin 5)	Output Y (Pin 6)
LOW	LOW	HIGH, 5.14 v
LOW	HIGH	HIGH, 5.14 v
HIGH	LOW	HIGH, 5.14 v
HIGH	HIGH	LOW, 0.00 v


Gate #3

Input A (Pin 10)	Input B (Pin 9)	Output Y (Pin 8)
LOW	LOW	HIGH, 5.14 v
LOW	HIGH	HIGH, 5.14 v
HIGH	LOW	HIGH, 5.14 v
HIGH	HIGH	LOW, 0.00 v

Gate #4

Input A (Pin 13)	Input B (Pin 12)	Output Y (Pin 11)
LOW	LOW	HIGH, 5.14 v
LOW	HIGH	HIGH, 5.14 v
HIGH	LOW	HIGH, 5.14 v
HIGH	HIGH	LOW, 0.00 v

74LS02 – Quad 2-input NOR Gate

 

Truth Tables:

Gate #1

Input A (Pin 2)	Input B (Pin 3)	Output Y (Pin 1)
LOW	LOW	HIGH, 5.11 v
LOW	HIGH	LOW, 0.00 v
HIGH	LOW	LOW, 0.00 v
HIGH	HIGH	LOW, 0.00 v

Gate #2

Input A (Pin 5)	Input B (Pin 6)	Output Y (Pin 4)
LOW	LOW	HIGH, 5.11 v
LOW	HIGH	LOW, 0.00 v
HIGH	LOW	LOW, 0.00 v
HIGH	HIGH	LOW, 0.00 v


Gate #3

Input A (Pin 9)	Input B (Pin 8)	Output Y (Pin 10)
LOW	LOW	HIGH, 5.11 v
LOW	HIGH	LOW, 0.00 v
HIGH	LOW	LOW, 0.00 v
HIGH	HIGH	LOW, 0.00 v

Gate #4

Input A (Pin 12)	Input B (Pin 11)	Output Y (Pin 13)
LOW	LOW	HIGH, 5.11 v
LOW	HIGH	LOW, 0.00 v
HIGH	LOW	LOW, 0.00 v
HIGH	HIGH	LOW, 0.00 v

74LS04 – Hex Inverters

 

Truth Tables:

Gate #1

Input A (Pin 1)	N/A	Output Y (Pin 2)
LOW	N/A	HIGH, 5.06 v
HIGH	N/A	LOW, 0.00 v

Gate #2

Input A (Pin 3)	N/A	Output Y (Pin 4)
LOW	N/A	HIGH, 5.06 v
HIGH	N/A	LOW, 0.00 v

Gate #3

Input A (Pin 5)	N/A	Output Y (Pin 6)
LOW	N/A	HIGH, 5.06 v
HIGH	N/A	LOW, 0.00 v

Gate #4

Input A (Pin 9)	N/A	Output Y (Pin 8)
LOW	N/A	HIGH, 5.06 v
HIGH	N/A	LOW, 0 v

Gate #5


Input A (Pin 11)	N/A	Output Y (Pin 10)
LOW	N/A	HIGH, 5.06 v
HIGH	N/A	LOW, 0.00 v

Gate #6

Input A (Pin 13)	N/A	Output Y (Pin 12)
LOW	N/A	HIGH, 5.06 v
HIGH	N/A	LOW, 0.00 v

74LS08 – Quad 2-input AND Gate

Pin Layout:

 

Truth Tables:

Gate #1

Input A (Pin 1)	Input B (Pin 2)	Output Y (Pin 3)
LOW	LOW	LOW, 0.00 v
LOW	HIGH	LOW, 0.00 v
HIGH	LOW	LOW, 0.00 v
HIGH	HIGH	HIGH, 5.16 v

Gate #2

Input A (Pin 4)	Input B (Pin 5)	Output Y (Pin 6)
LOW	LOW	LOW, 0.00 v
LOW	HIGH	LOW, 0.00 v
HIGH	LOW	LOW, 0.00 v
HIGH	HIGH	HIGH, 5.16 v


Gate #3

Input A (Pin 9)	Input B (Pin 10)	Output Y (Pin 8)
LOW	LOW	LOW, 0.00 v
LOW	HIGH	LOW, 0.00 v
HIGH	LOW	LOW, 0.00 v
HIGH	HIGH	HIGH, 5.16 v

Gate #4

Input A (Pin 12)	Input B (Pin 13)	Output Y (Pin 11)
LOW	LOW	LOW, 0.00 v
LOW	HIGH	LOW, 0.00 v
HIGH	LOW	LOW, 0.00 v
HIGH	HIGH	HIGH, 5.16 v

74LS11 – Triple 3-input AND Gate

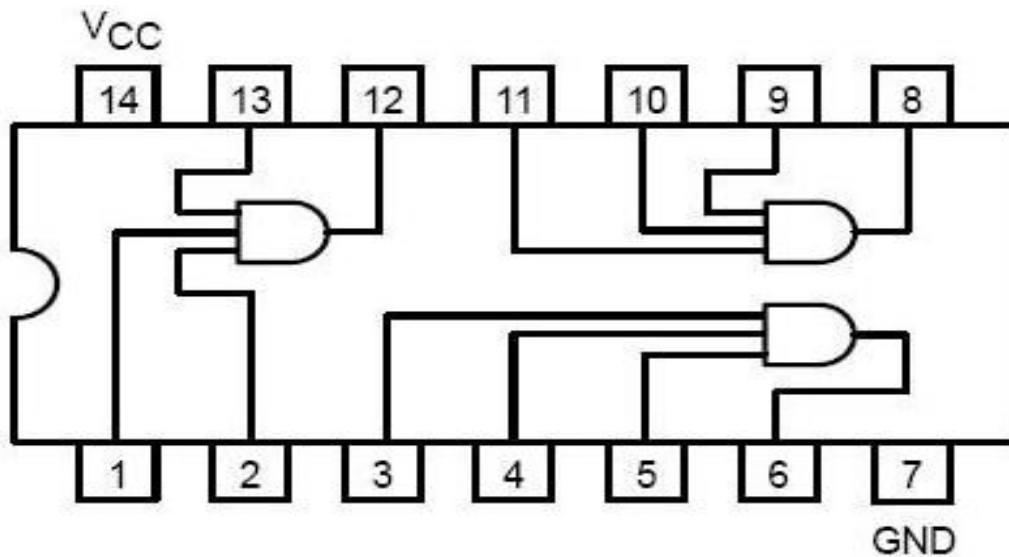

Truth Tables:

Gate #1

Input A (Pin 1)	Input B (Pin 2)	Input C (Pin 13)	Output Y (Pin 12)
LOW	LOW	LOW	LOW, 0.00 v
LOW	LOW	HIGH	LOW, 0.00 v
LOW	HIGH	LOW	LOW, 0.00 v
LOW	HIGH	HIGH	LOW, 0.00 v
HIGH	LOW	LOW	LOW, 0.00 v
HIGH	LOW	HIGH	LOW, 0.00 v
HIGH	HIGH	LOW	LOW, 0.00 v
HIGH	HIGH	HIGH	HIGH, 5.12 v


Gate #2

Input A (Pin 3)	Input B (Pin 4)	Input C (Pin 5)	Output Y (Pin 6)
LOW	LOW	LOW	LOW, 0.00 v
LOW	LOW	HIGH	LOW, 0.00 v
LOW	HIGH	LOW	LOW, 0.00 v
LOW	HIGH	HIGH	LOW, 0.00 v
HIGH	LOW	LOW	LOW, 0.00 v
HIGH	LOW	HIGH	LOW, 0.00 v
HIGH	HIGH	LOW	LOW, 0.00 v
HIGH	HIGH	HIGH	HIGH, 5.12 v

Gate #3

Input A (Pin 11)	Input B (Pin 10)	Input C (Pin 9)	Output Y (Pin 8)
LOW	LOW	LOW	LOW, 0.00 v
LOW	LOW	HIGH	LOW, 0.00 v
LOW	HIGH	LOW	LOW, 0.00 v
LOW	HIGH	HIGH	LOW, 0.00 v
HIGH	LOW	LOW	LOW, 0.00 v
HIGH	LOW	HIGH	LOW, 0.00 v
HIGH	HIGH	LOW	LOW, 0.00 v
HIGH	HIGH	HIGH	HIGH, 5.12 v

74LS32 – Quad 2-input OR Gate

 

Truth Tables:

Gate #1

Input A (Pin 1)	Input B (Pin 2)	Output Y (Pin 3)
LOW	LOW	LOW, 0.00 v
LOW	HIGH	HIGH, 5.13 v
HIGH	LOW	HIGH, 5.13 v
HIGH	HIGH	HIGH, 5.13 v

Gate #2

Input A (Pin 4)	Input B (Pin 5)	Output Y (Pin 6)
LOW	LOW	LOW, 0.00 v
LOW	HIGH	HIGH, 5.13 v
HIGH	LOW	HIGH, 5.13 v
HIGH	HIGH	HIGH, 5.13 v


Gate #3

Input A (Pin 10)	Input B (Pin 9)	Output Y (Pin 8)
LOW	LOW	LOW, 0.00 v
LOW	HIGH	HIGH, 5.13 v
HIGH	LOW	HIGH, 5.13 v
HIGH	HIGH	HIGH, 5.13 v

Gate #4

Input A (Pin 13)	Input B (Pin 12)	Output Y (Pin 11)
LOW	LOW	LOW, 0.00 v
LOW	HIGH	HIGH, 5.13 v
HIGH	LOW	HIGH, 5.13 v
HIGH	HIGH	HIGH, 5.13 v

74LS86 – Quad 2-input XOR Gate

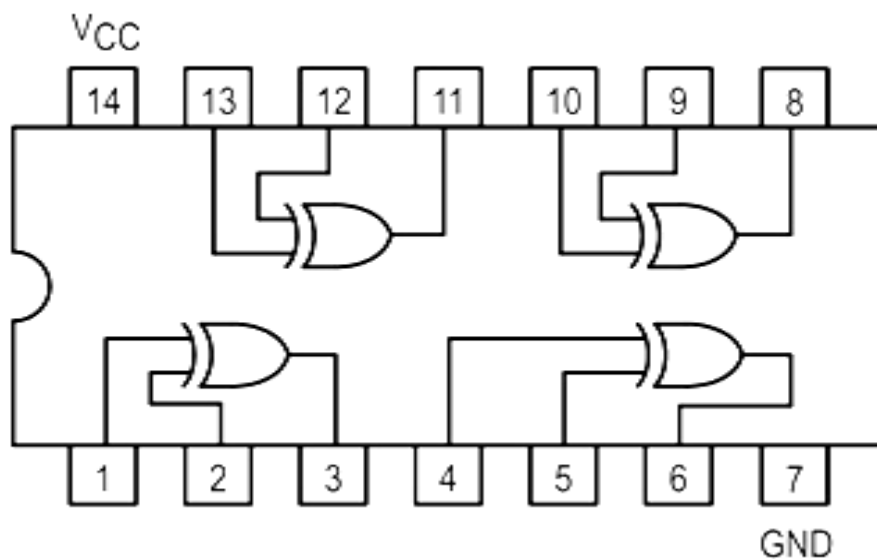

Truth Tables:

Gate #1

Input A (Pin 1)	Input B (Pin 2)	Output Y (Pin 3)
LOW	LOW	LOW, 0.00 v
LOW	HIGH	HIGH, 5.13 v
HIGH	LOW	HIGH, 5.13 v
HIGH	HIGH	LOW, 0.00 v

Gate #2

Input A (Pin 4)	Input B (Pin 5)	Output Y (Pin 6)
LOW	LOW	LOW, 0.00 v
LOW	HIGH	HIGH, 5.13 v
HIGH	LOW	HIGH, 5.13 v
HIGH	HIGH	LOW, 0.00 v


Gate #3

Input A (Pin 10)	Input B (Pin 9)	Output Y (Pin 8)
LOW	LOW	LOW, 0.00 v
LOW	HIGH	HIGH, 5.13 v
HIGH	LOW	HIGH, 5.13 v
HIGH	HIGH	LOW, 0.00 v

Gate #4

Input A (Pin 13)	Input B (Pin 12)	Output Y (Pin 11)
LOW	LOW	LOW, 0.00 v
LOW	HIGH	HIGH, 5.13 v
HIGH	LOW	HIGH, 5.13 v
HIGH	HIGH	LOW, 0.00 v

 74LS03 – Quad 2-input NAND Gate with Open Collector Outputs



Truth Tables:

Gate #1

Input A (Pin 1)	Input B (Pin 2)	Output Y (Pin 3)
LOW	LOW	N/C
LOW	HIGH	N/C
HIGH	LOW	N/C
HIGH	HIGH	LOW, 0.00 v

Gate #2 This is the truth table corresponding to the photo below.


Input A (Pin 4)	Input B (Pin 5)	Output Y (Pin 6)
LOW	LOW	N/C
LOW	HIGH	N/C
HIGH	LOW	N/C
HIGH	HIGH	LOW, 0.00 v

Gate #3

Input A (Pin 10)	Input B (Pin 9)	Output Y (Pin 8)
LOW	LOW	N/C
LOW	HIGH	N/C
HIGH	LOW	N/C
HIGH	HIGH	LOW, 0.00 v

Gate #4

Input A (Pin 13)	Input B (Pin 12)	Output Y (Pin 11)
LOW	LOW	N/C
LOW	HIGH	N/C
HIGH	LOW	N/C
HIGH	HIGH	LOW, 0.00 v

 

Truth Tables With 2k Pullup Resistor:

Gate #1

Input A (Pin 1)	Input B (Pin 2)	Output Y (Pin 3)
LOW	LOW	HIGH, 5.15 v
LOW	HIGH	HIGH, 5.15 v
HIGH	LOW	HIGH, 5.15 v
HIGH	HIGH	LOW, 0.03 v

Gate #2

Input A (Pin 4)	Input B (Pin 5)	Output Y (Pin 6)
LOW	LOW	HIGH, 5.15 v
LOW	HIGH	HIGH, 5.15 v
HIGH	LOW	HIGH, 5.15 v
HIGH	HIGH	LOW, 0.03 v

Gate #3

Input A (Pin 10)	Input B (Pin 9)	Output Y (Pin 8)
LOW	LOW	HIGH, 5.15 v
LOW	HIGH	HIGH, 5.15 v
HIGH	LOW	HIGH, 5.15 v
HIGH	HIGH	LOW, 0.03 v

Gate #4

Input A (Pin 13)	Input B (Pin 12)	Output Y (Pin 11)
LOW	LOW	HIGH, 5.15 v
LOW	HIGH	HIGH, 5.15 v
HIGH	LOW	HIGH, 5.15 v
HIGH	HIGH	LOW, 0.04 v